
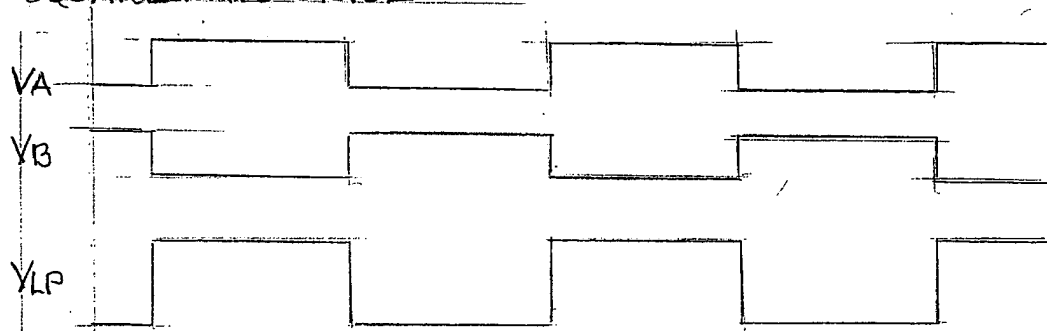


A) SQUARE WAVE DRIVE

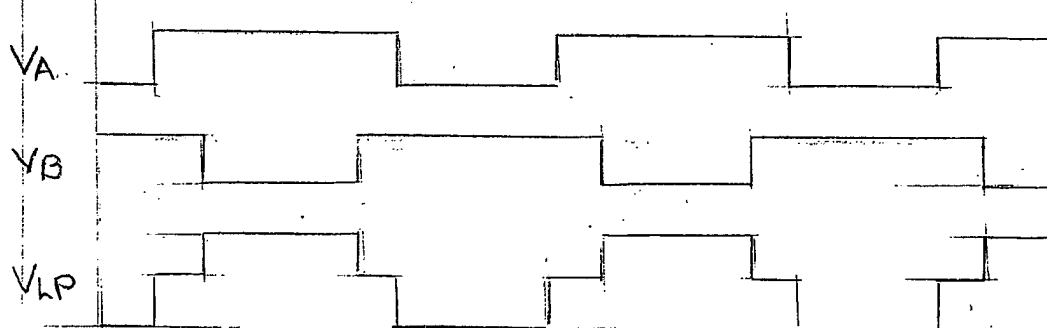

B) HIGH EFFICIENCY DRIVE



*Fig 2*

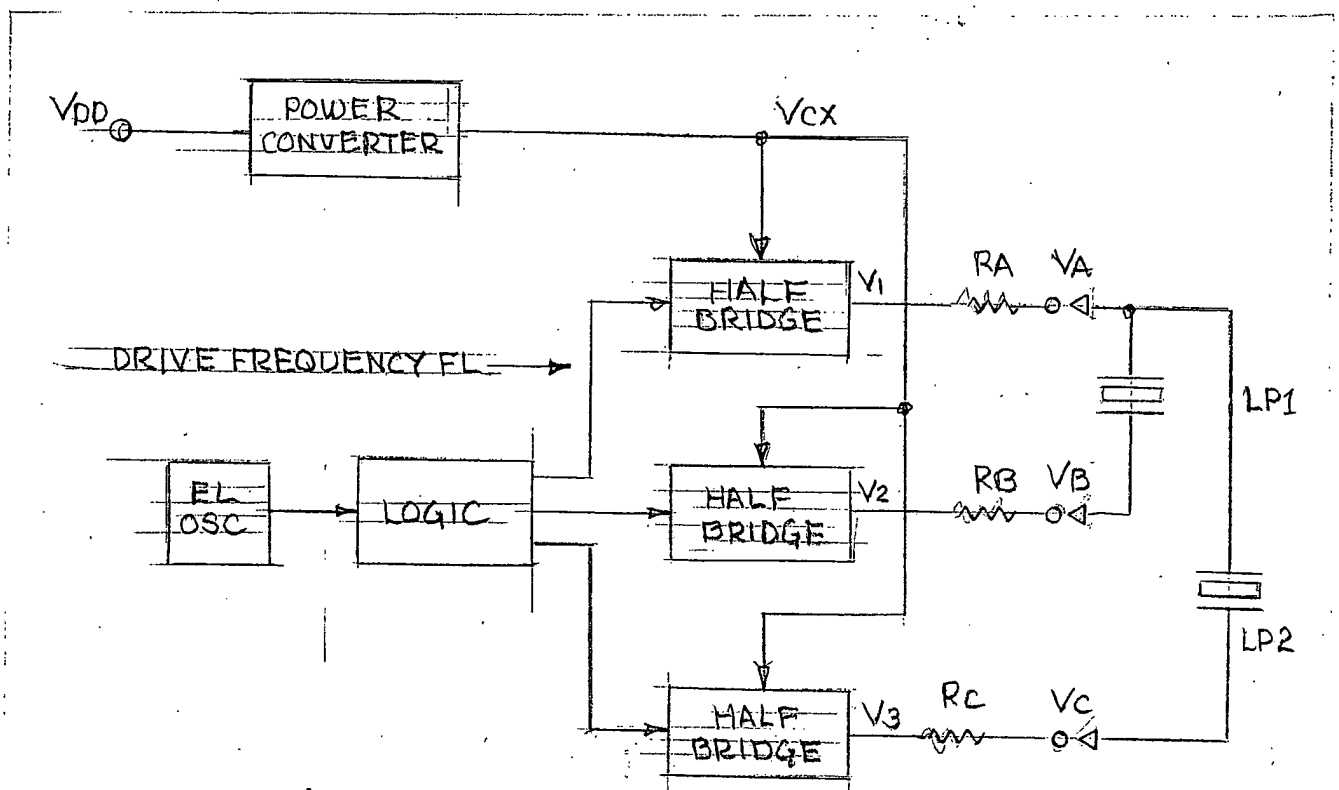


FIG. 3 MULTIPLE OUTPUT EL LAMP DRIVER

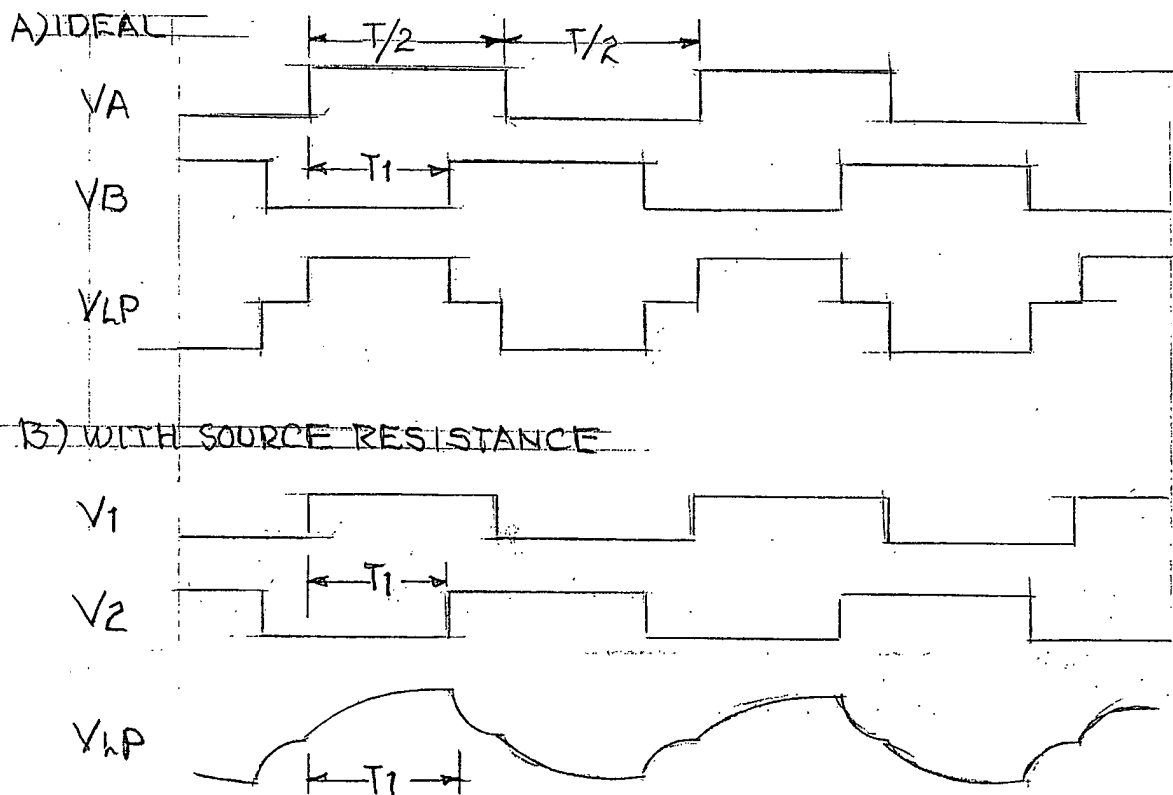


FIG. 4 PHASE SHIFTED DRIVE WAVEFORMS

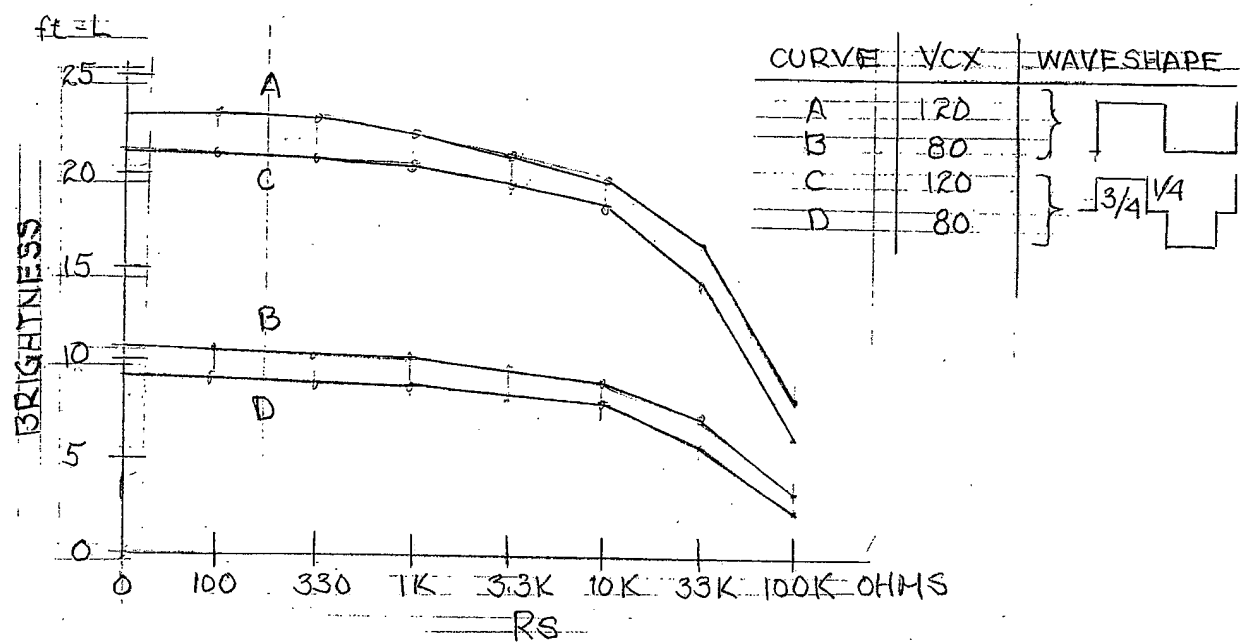


FIG. 5 LAMP BRIGHTNESS VS SERIES RESISTANCE  $R_s$

$F = 500 \text{ Hz}$  19X50mm LAMP

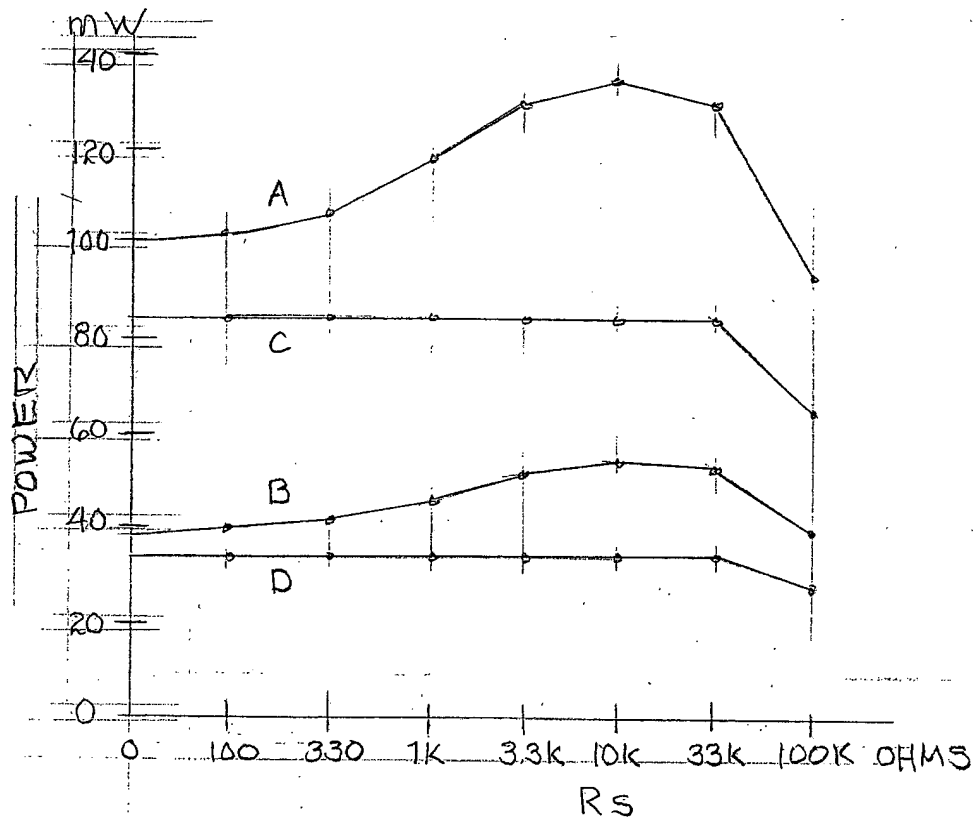


FIG. 6 LAMP POWER VS SERIES RESISTANCE

$F = 500 \text{ Hz}$  19X50 mm LAMP

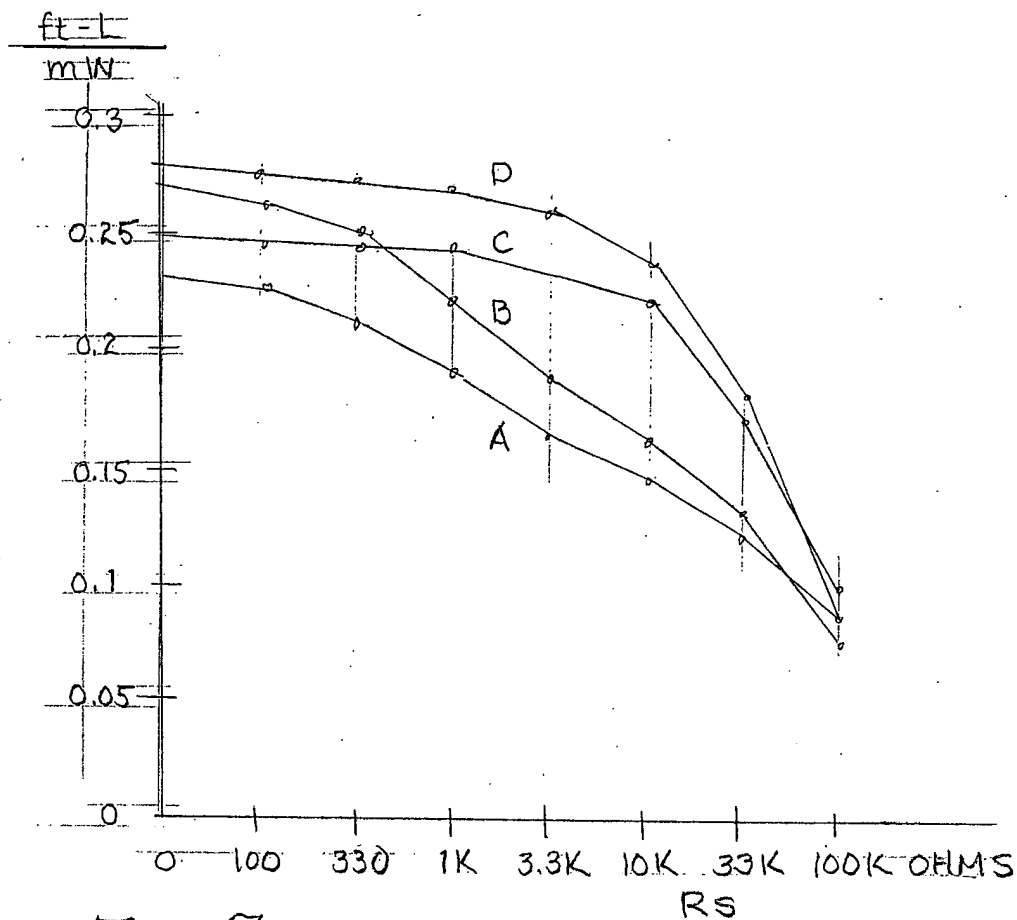


FIG. 7 LAMP EFFICIENCY VS SERIES RESISTANCE  
F = 500 HZ 19 x 50 mm LAMP

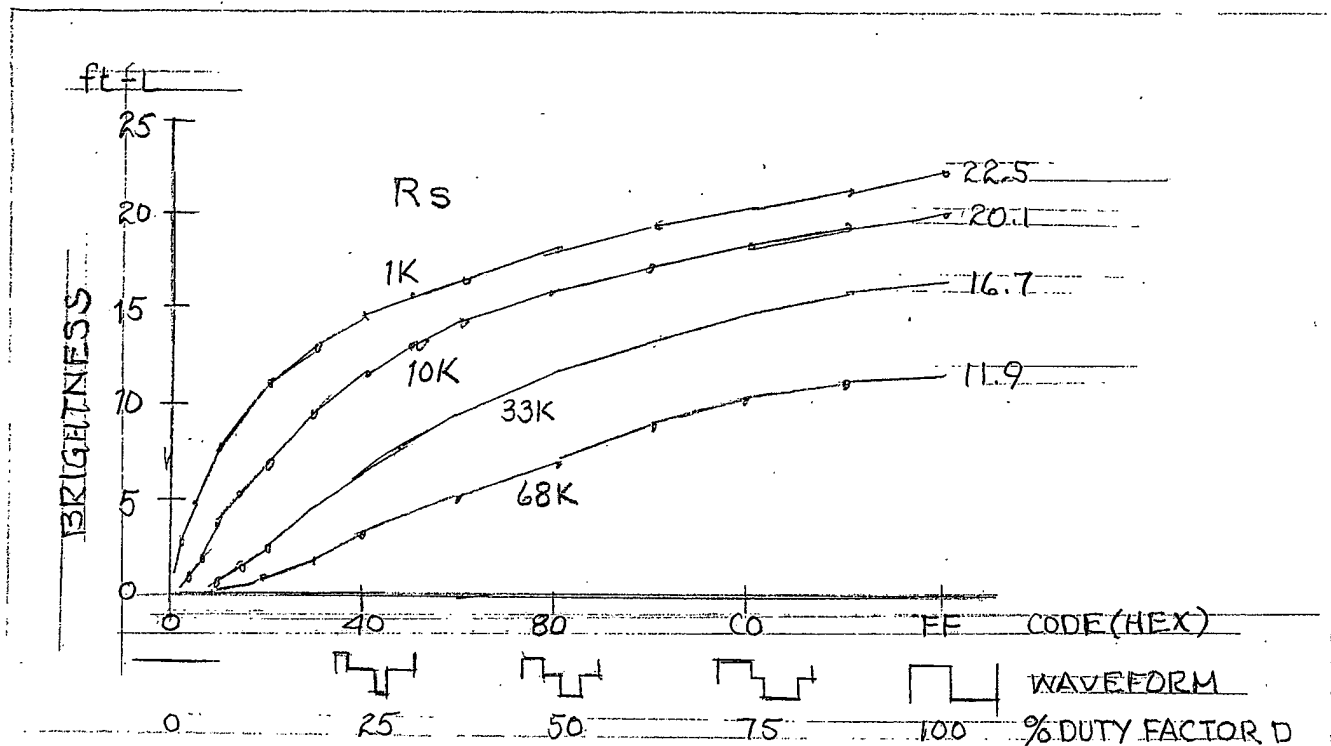


FIG. 8 LAMP BRIGHTNESS VS DUTY FACTOR

$V_{CX} = +120$   $F = 500 \text{ Hz}$  19X50 MM LAMP

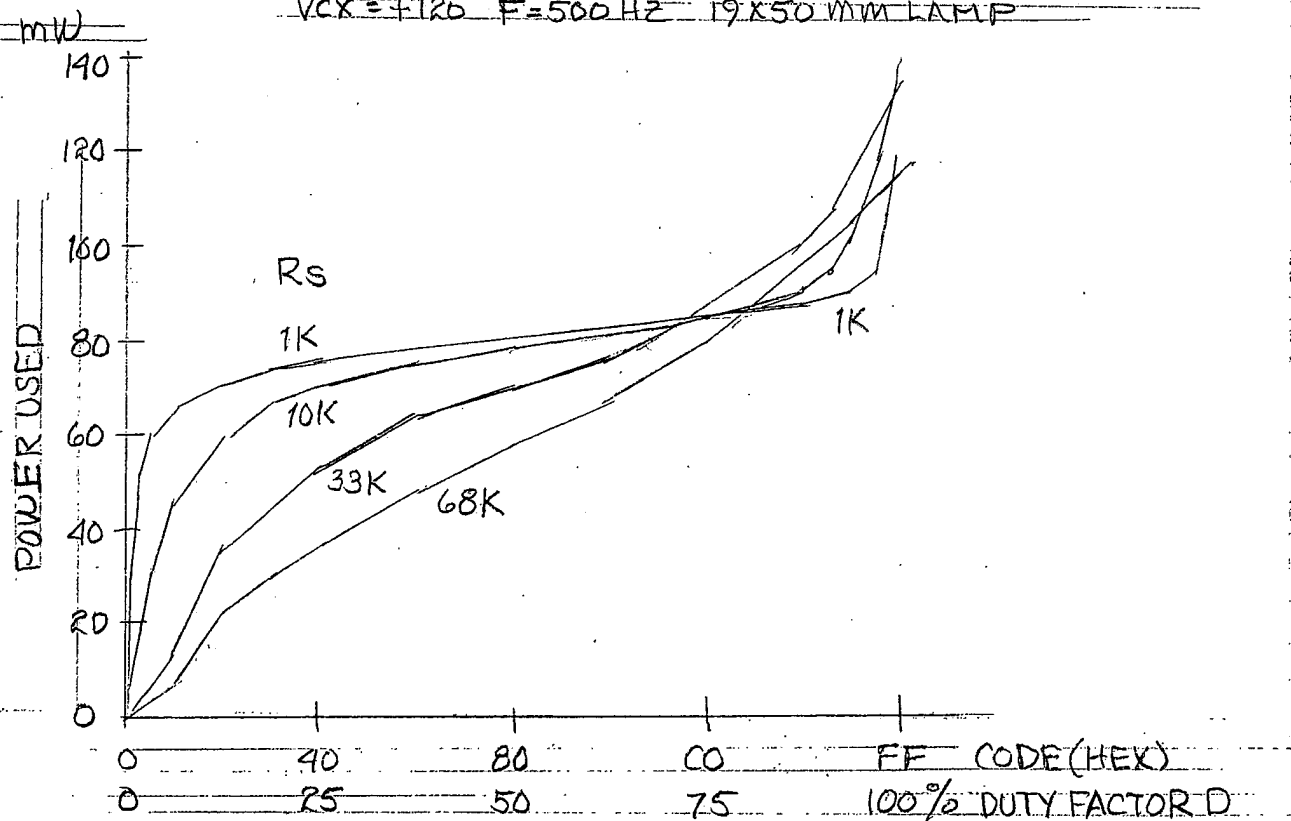


FIG. 9 LAMP POWER VS DUTY FACTOR

$V_{CX} = +120$   $F = 500 \text{ Hz}$  19X50mm LAMP

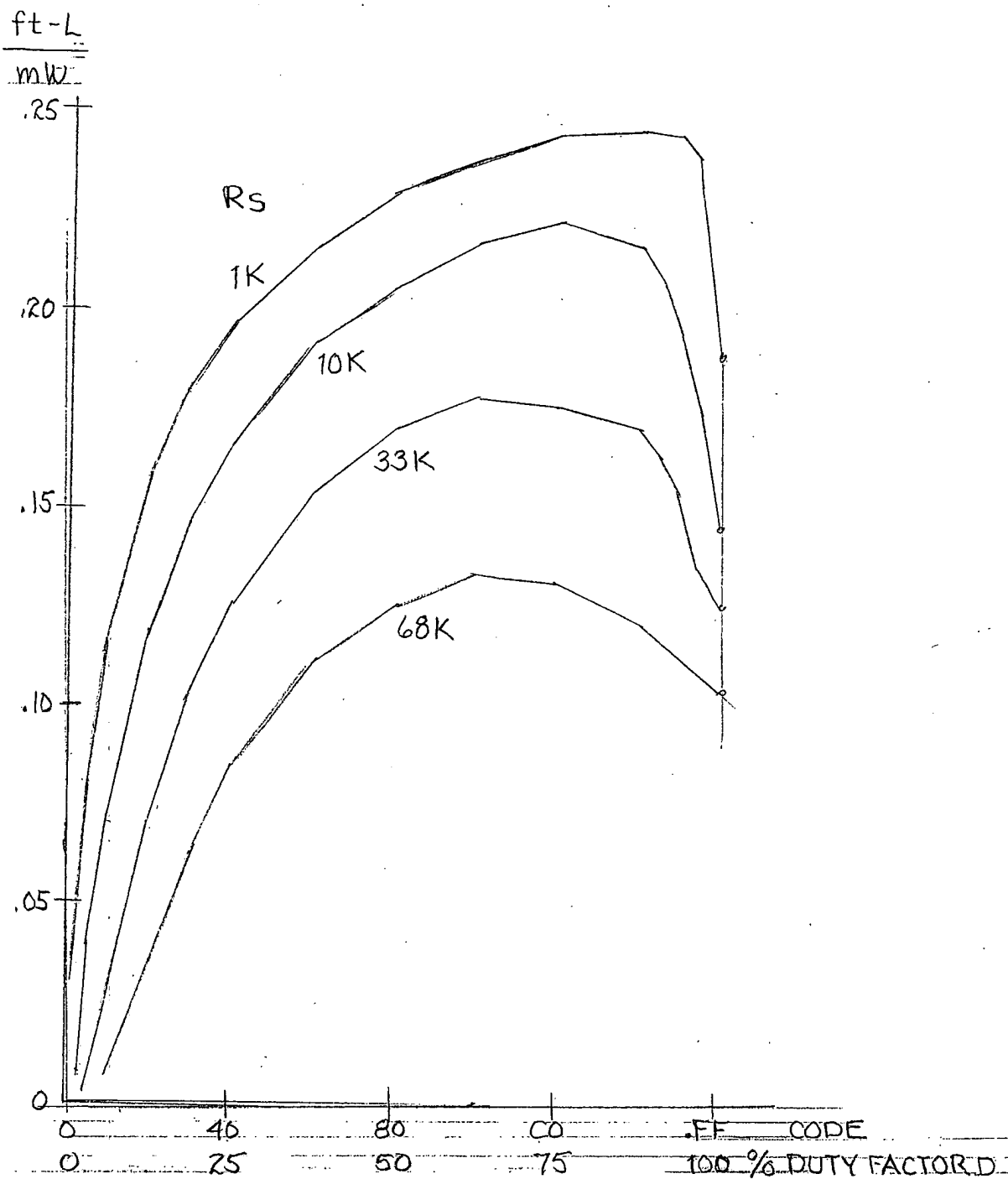


FIG. 10 LAMP EFFICIENCY VS DUTY FACTOR

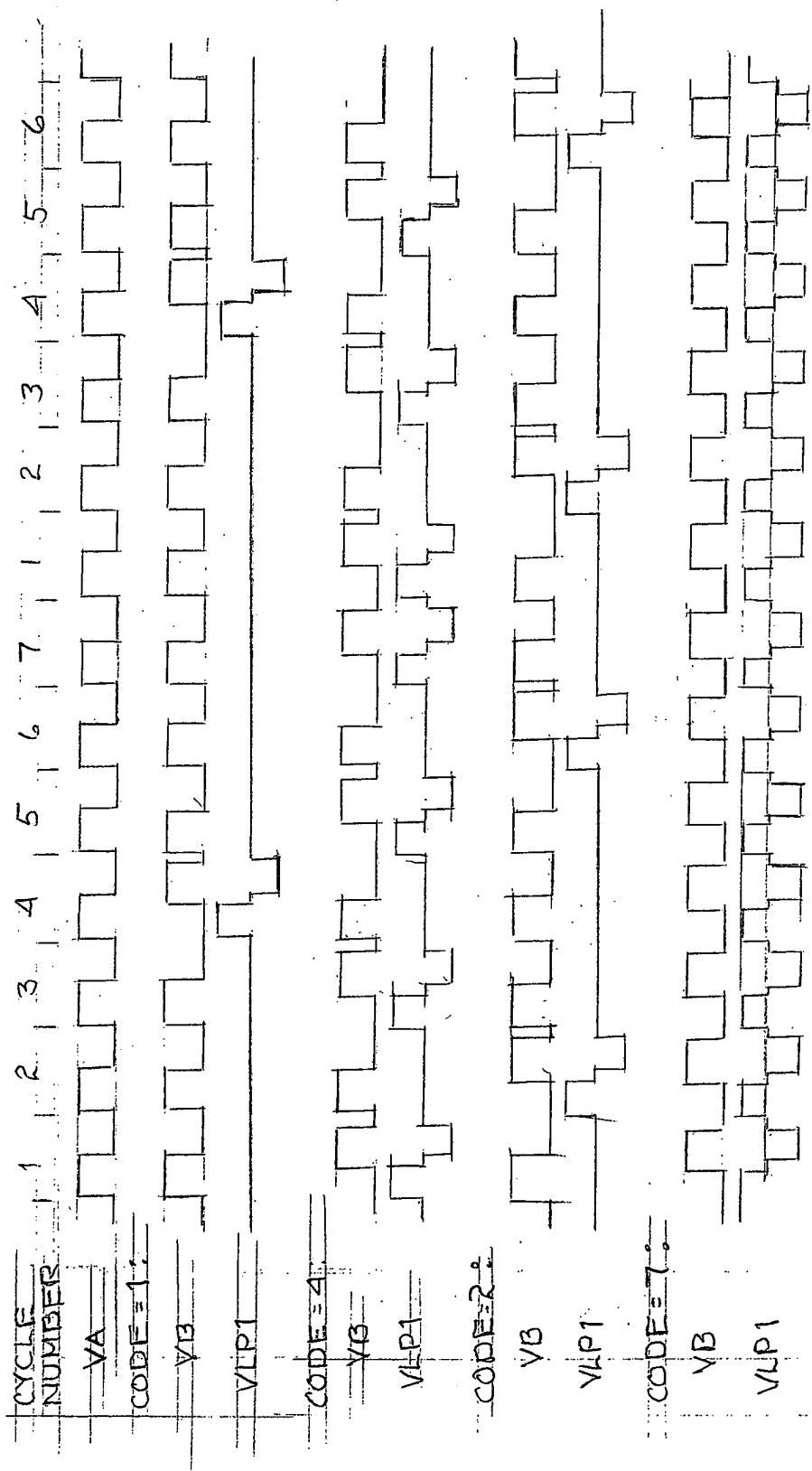


Fig. 11 AVERAGE FREQUENCY CONTROL

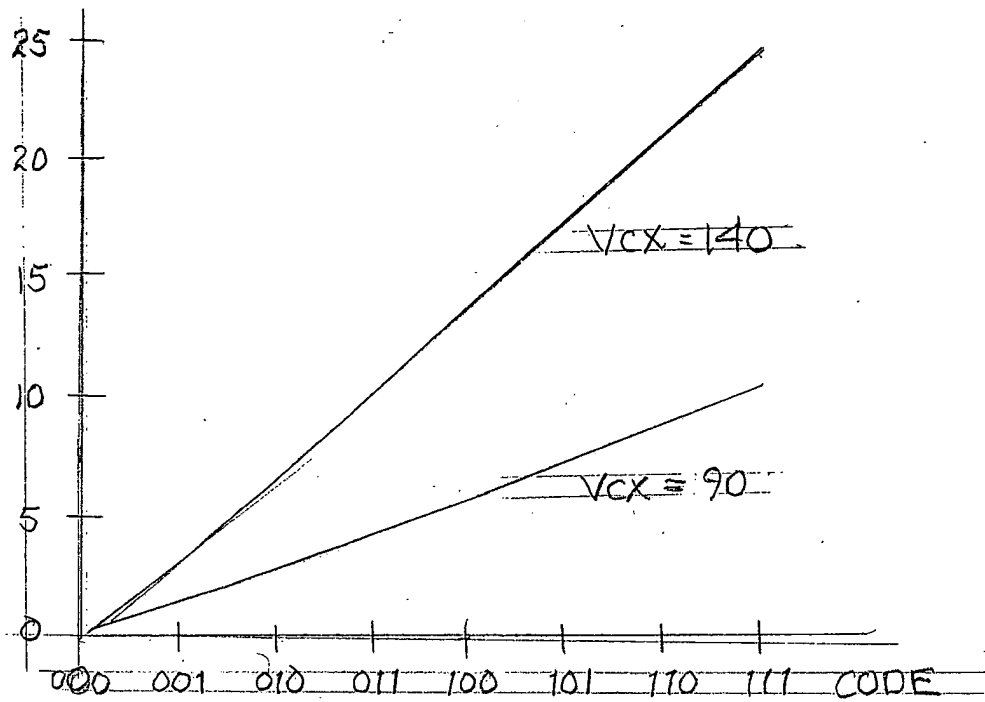


FIG 12 METHOD 2 - BRIGHTNESS

$F = 500 \text{ Hz}$  19x50 mm LAMP

$R_S = 3.3 \text{ K}\Omega$  3/4 DUTY PULSES

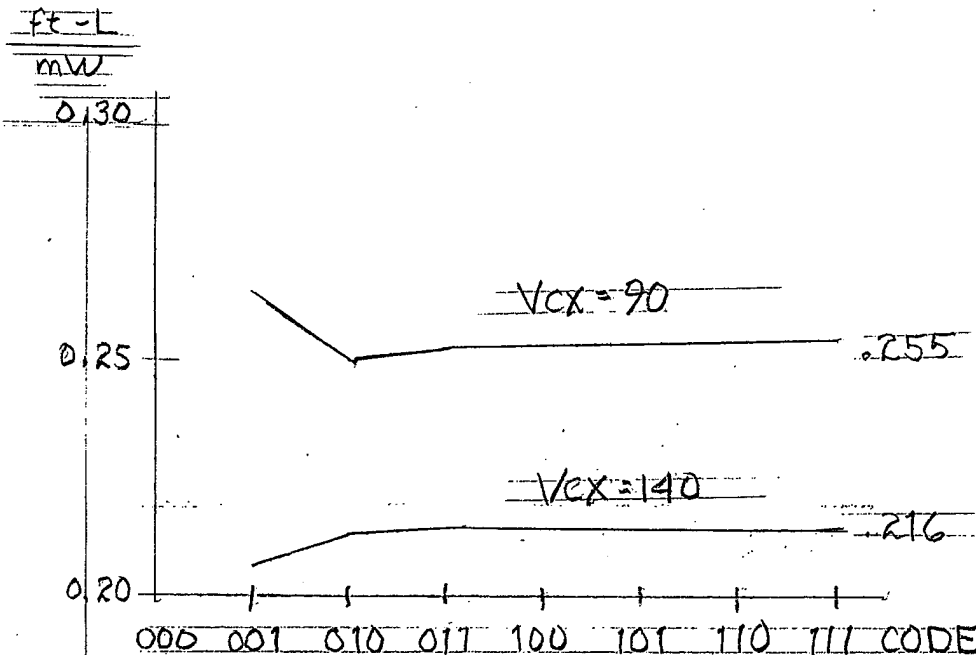


FIG 13 METHOD 2 EFFICIENCY



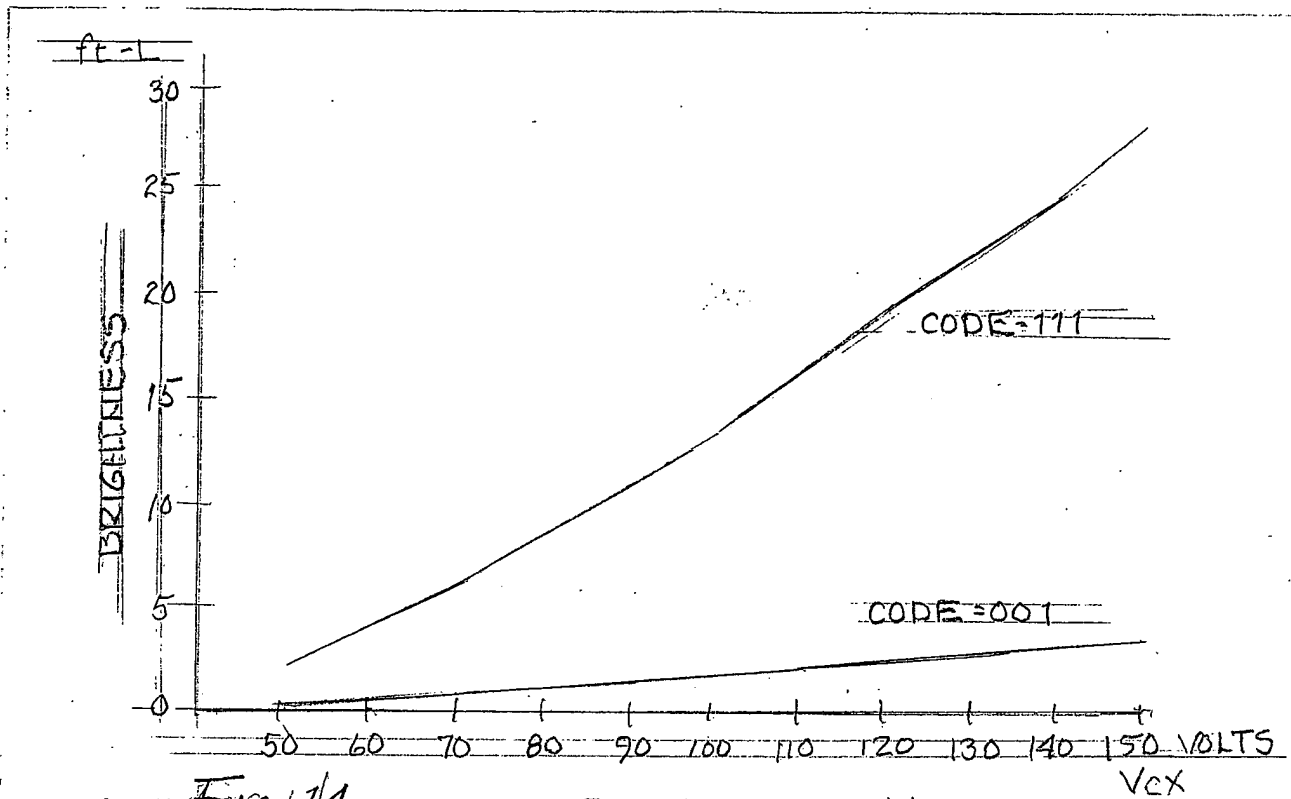


FIG. 14 METHOD 2 BRIGHTNESS VS V<sub>CX</sub>  
 $F=500\text{ Hz}$  19X50 MM LAMP  
 $R_S=3.3\text{ K}$  3/4, 1/4 DUTY PULSES

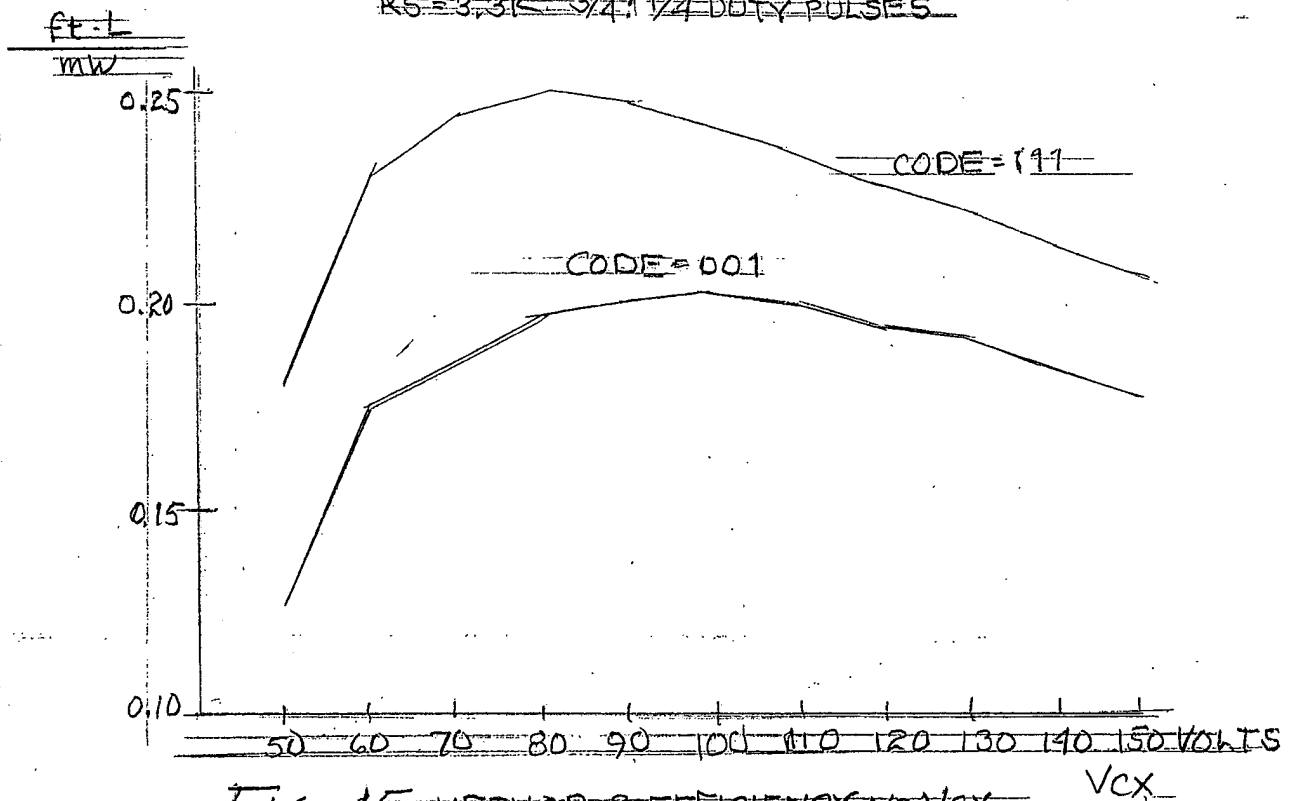


FIG. 15 METHOD 2 EFFICIENCY VS V<sub>CX</sub>  
 $F=500\text{ Hz}$  19X50 MM LAMP  
 $R_S=3.3\text{ K}$  3/4, 1/4 DUTY PULSES

$f_t = 1$

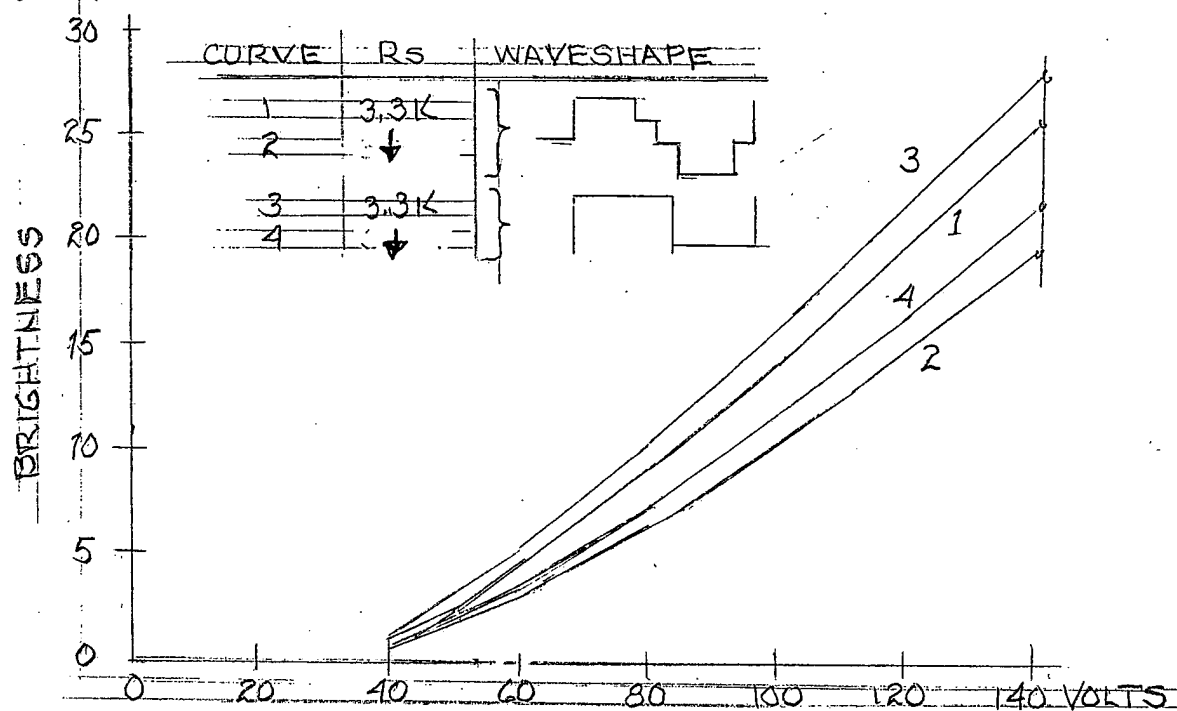


FIG. 16 LAMP BRIGHTNESS VS  $V_{CX}$   
 $F = 500 \text{ Hz}$  19X50MM LAMP

$f_t = 1$   
 mw

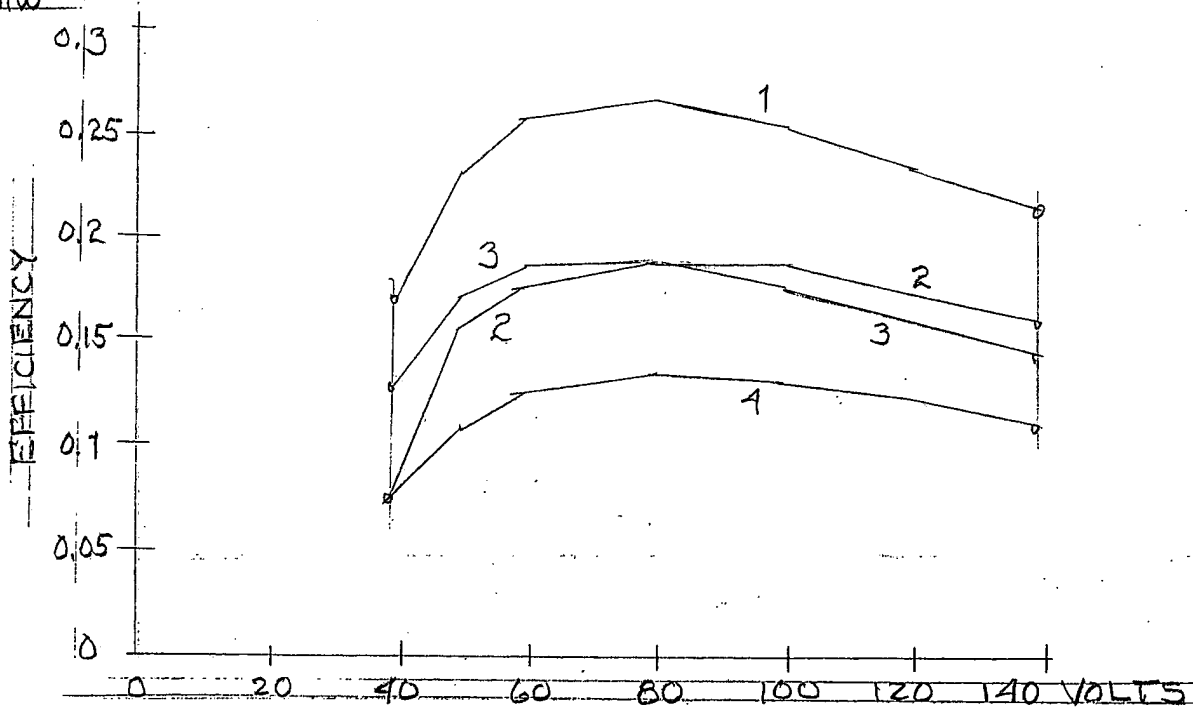


FIG. 17 LAMP EFFICIENCY VS  $V_{CX}$   
 $F = 500 \text{ Hz}$  19X50MM LAMP


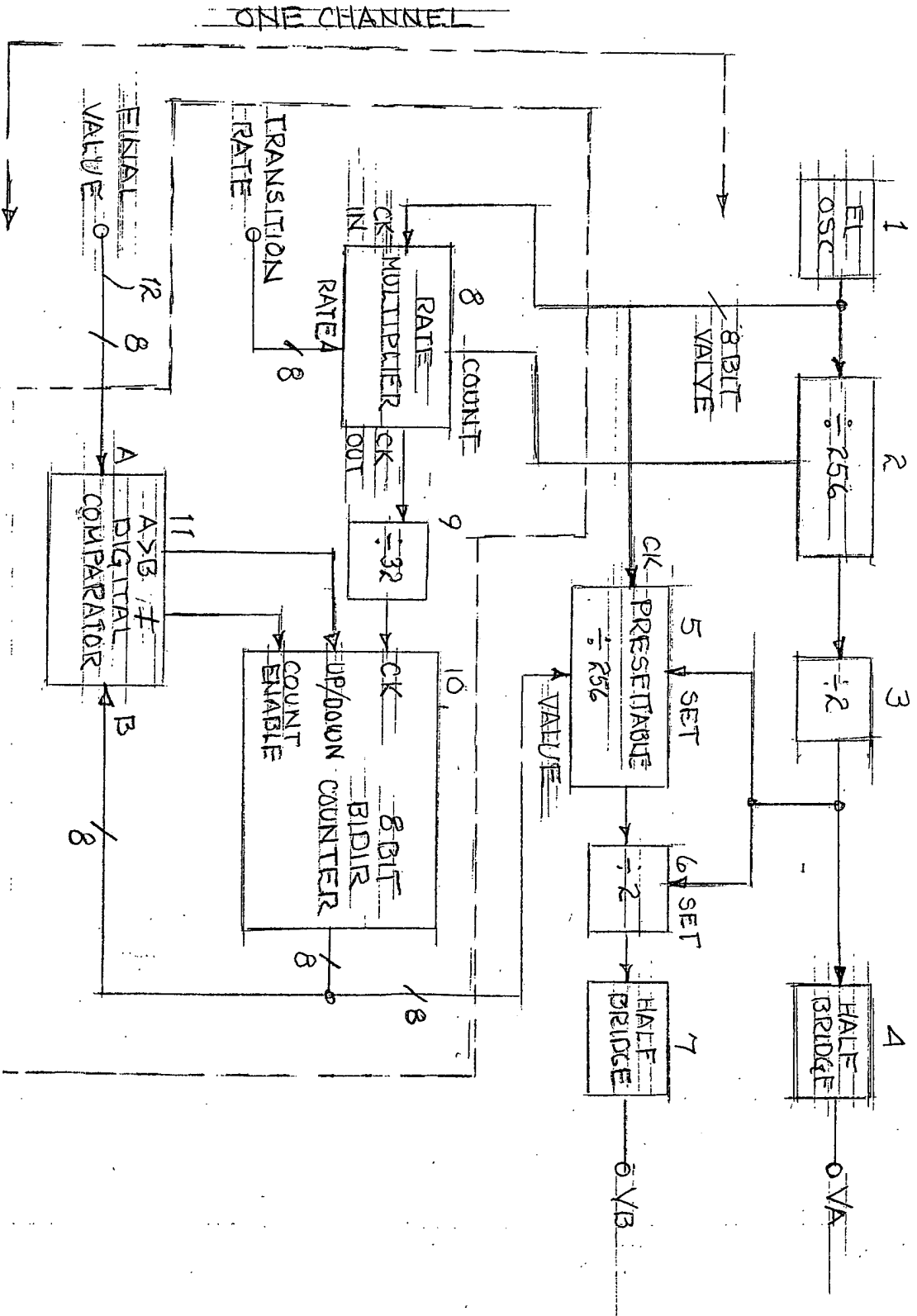


Fig. 18 VARIABLE TRANSITION RATE PHASE CONTROL

ADDED FOR TRANSITION RATE CONTROL

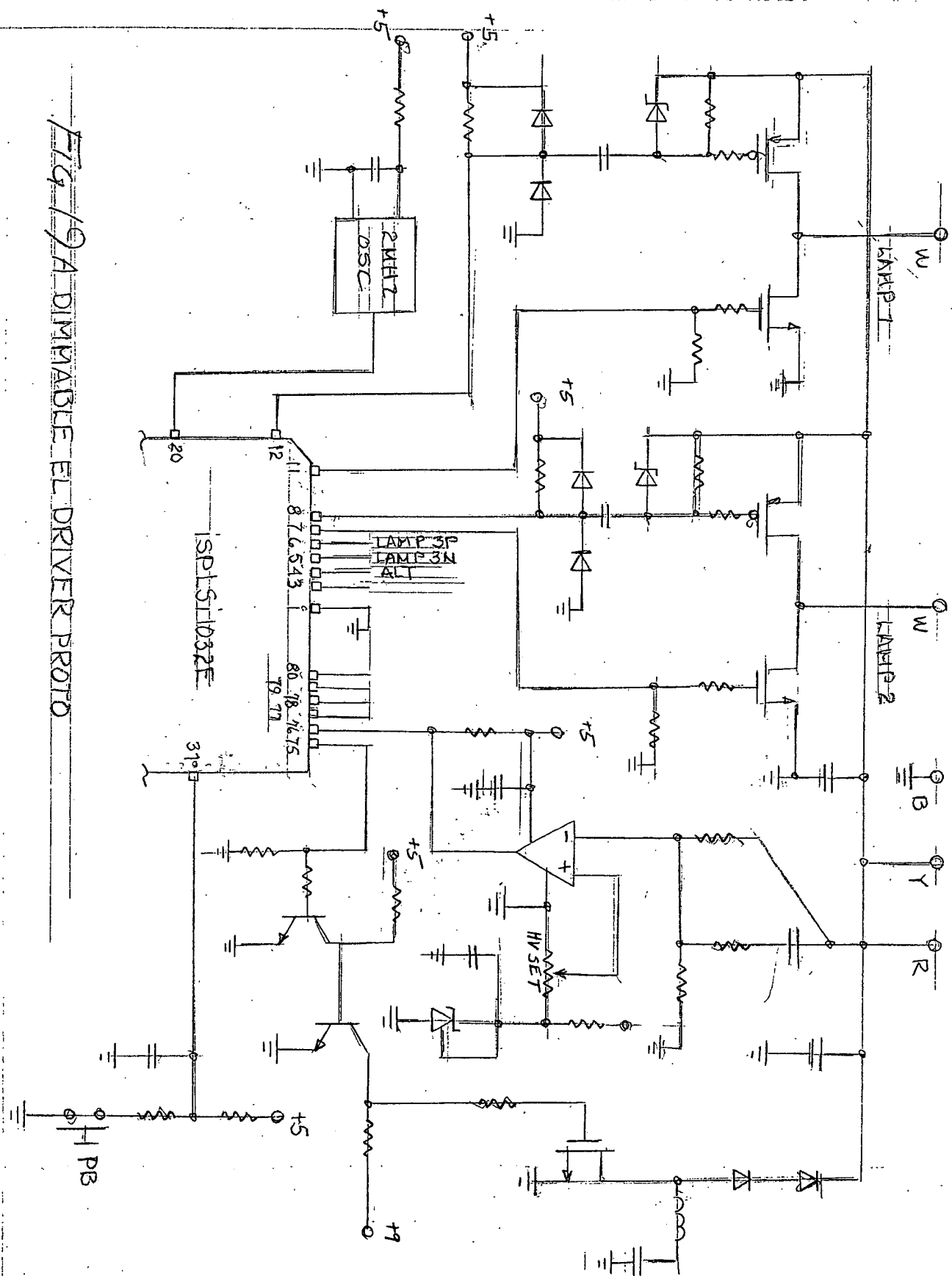

7/19/94 DIMMABLE EL DRIVER PROTO

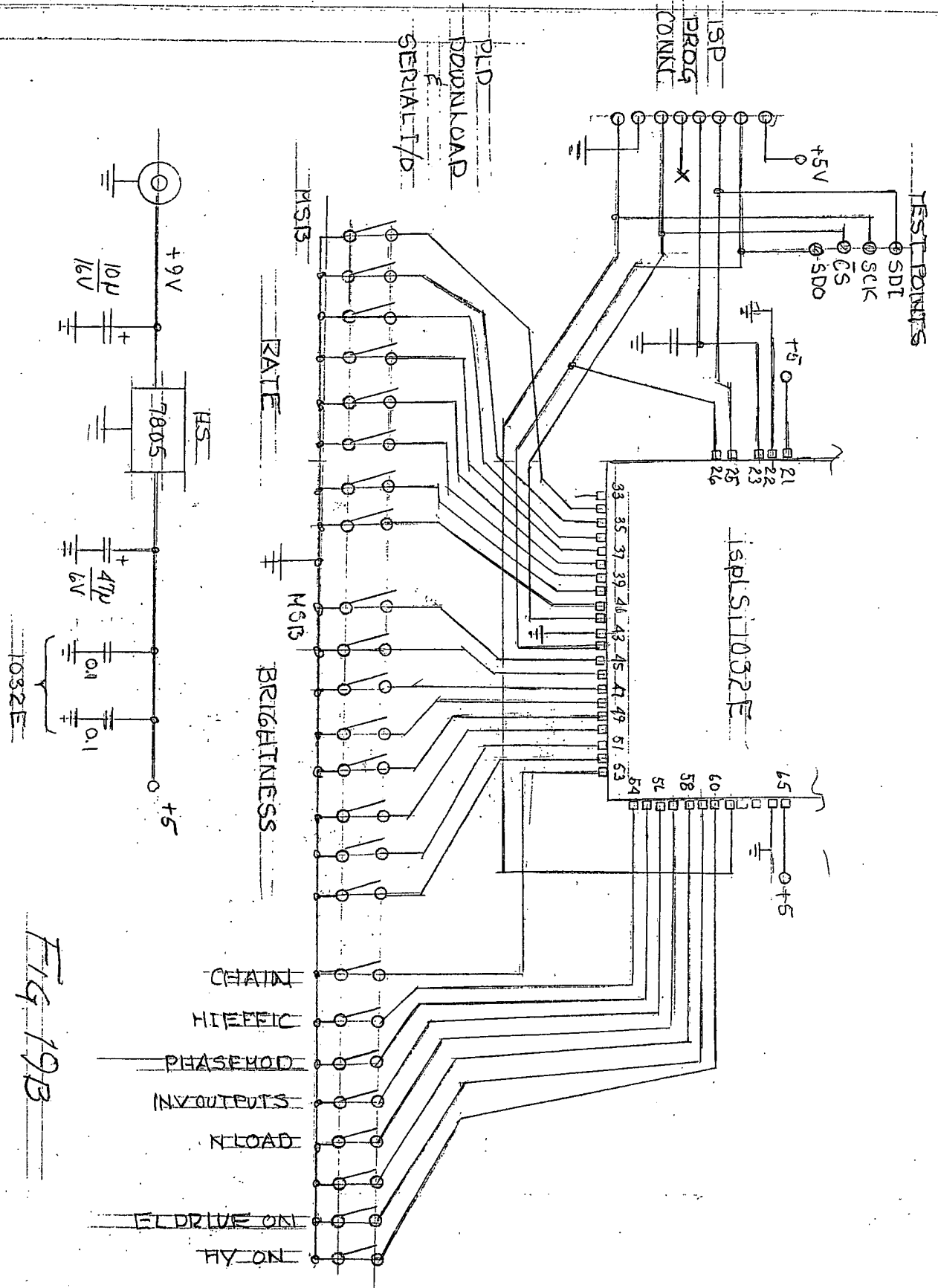


Fig 19B